


MPSL2019

Lab3


Components of lab

- Breadboard
- 4DIP Switch
- 1K Ω Network Resistor *1
- LED *4
- 220 Ω resistor *4

Breadboard

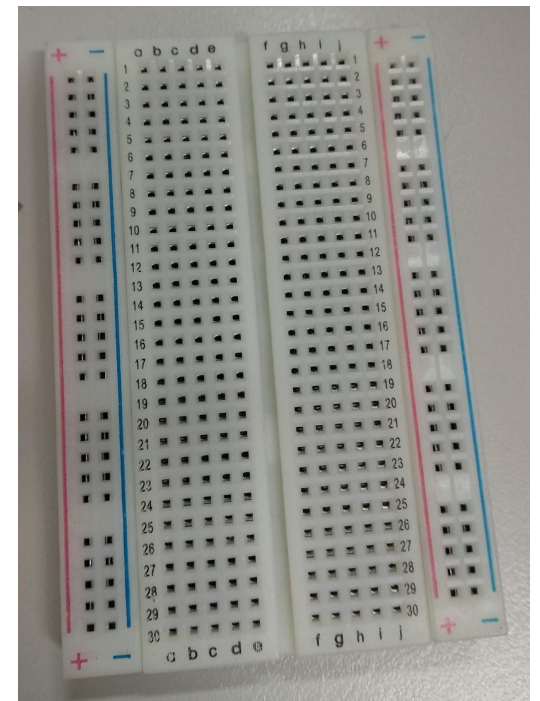

4 DIP Switch

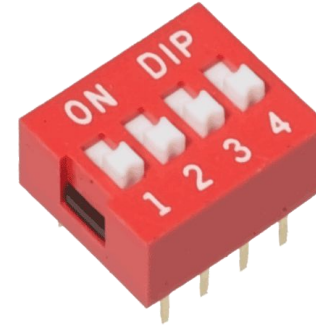

1k Ω Network resistor



LED * 4



220 Ω resistor *4




Breadboard

- Easy to connect electronic components
- Please be careful when plugging and unplugging



vertical
connec
tion

直向相通

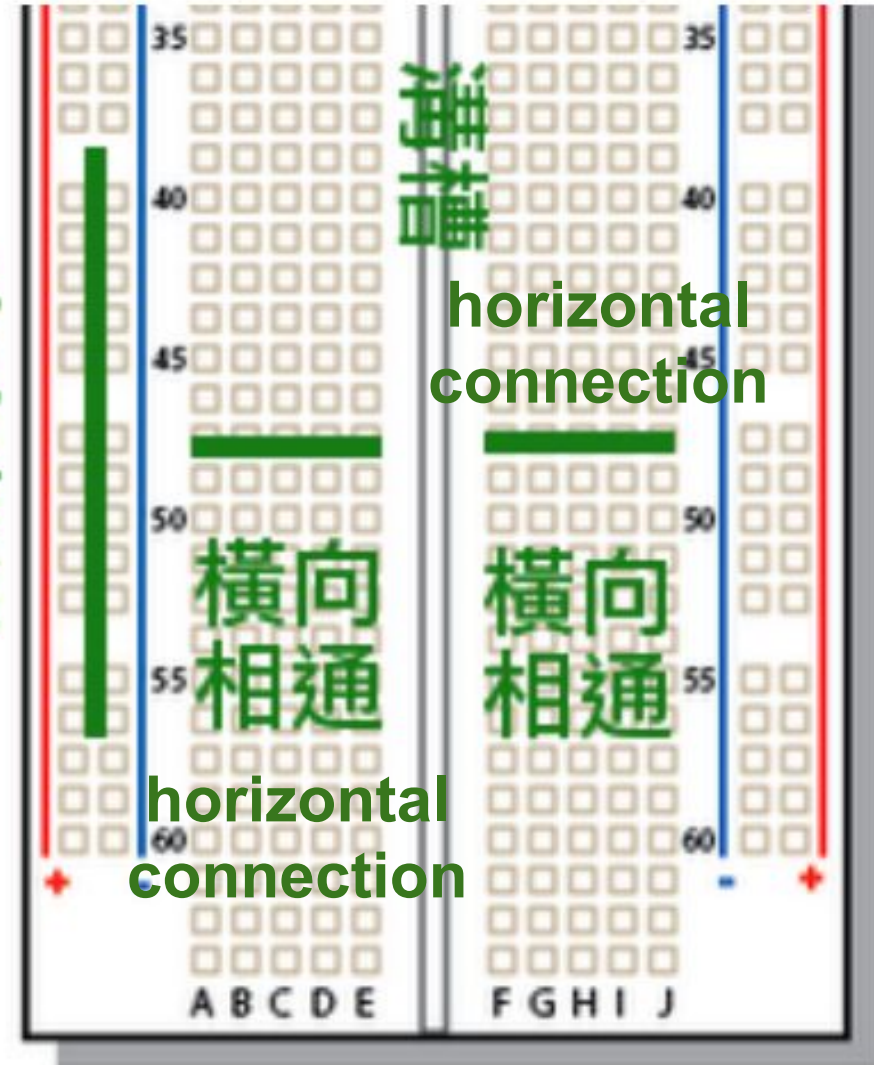

Resistor and LED

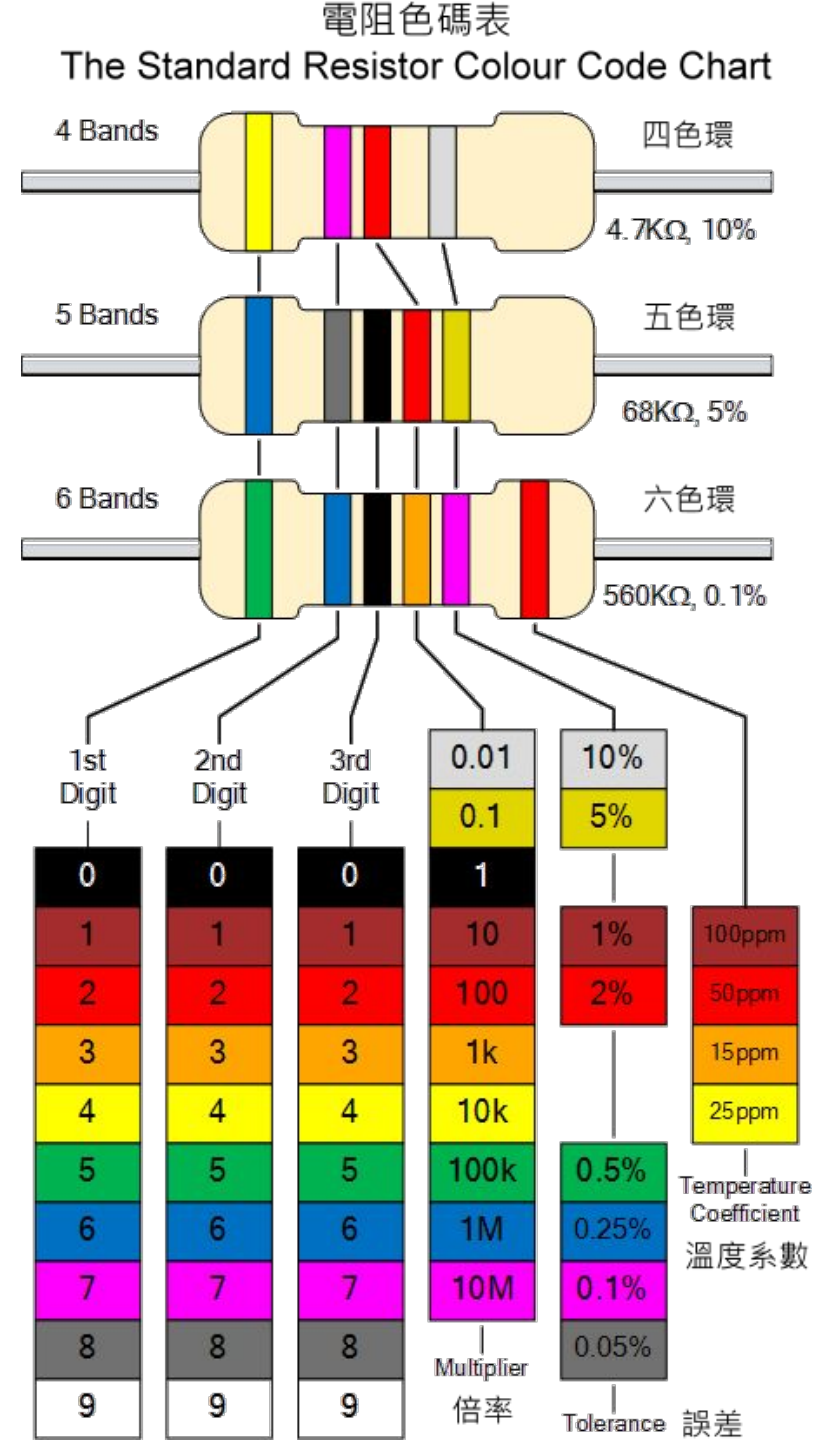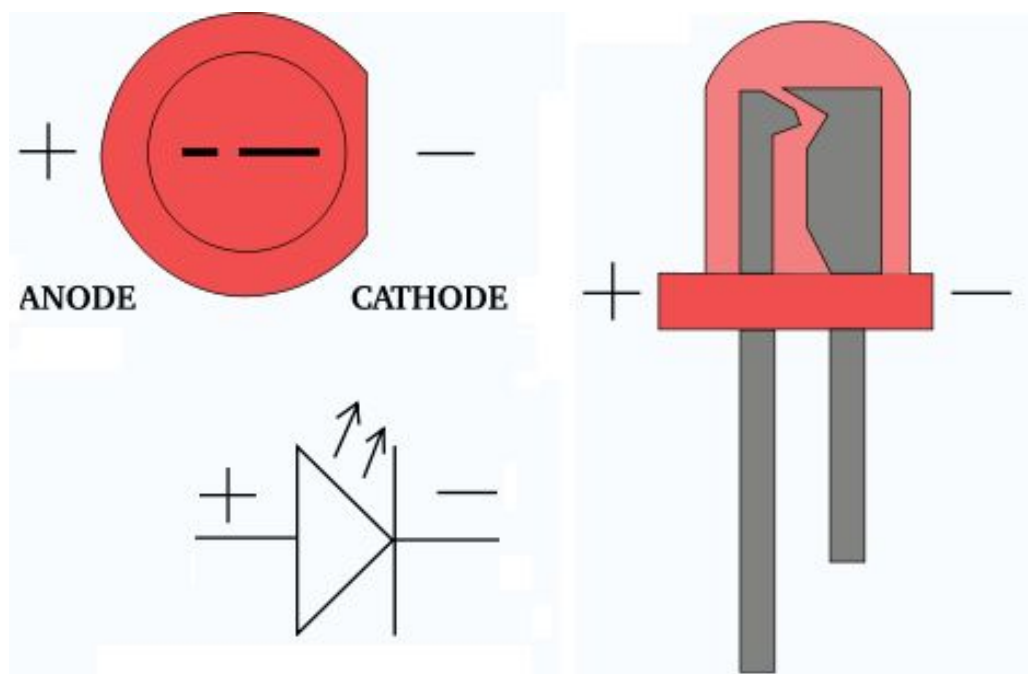- mark resistor value by colour code
- the long pin of LED is positive (+)




Network resistor 排列電阻



- many resistors in it
- mark resistor value by number, e.g : $102=10*10^2 = 1K \Omega$

network resistor naming			
circuit type	number of pins	resistor value	difference
<ul style="list-style-type: none">• A : all resistors share one pin (leftmost)• B : each resistor has its own independent pin• ...	4 ~ 14	three-digital first and second digital are valid number and third digital is number of zero after valid number	<ul style="list-style-type: none">• F : $\pm 1\%$• G : $\pm 2\%$• J : $\pm 5\%$

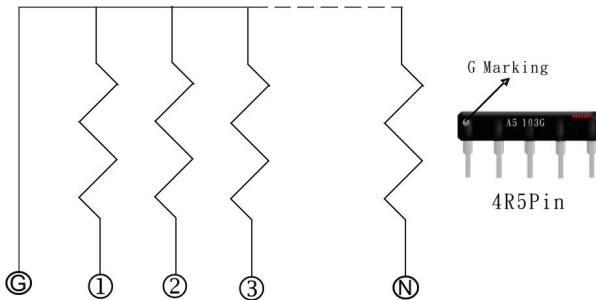直立式排列電阻 A 電路
Network Resistor Circuit - A Type



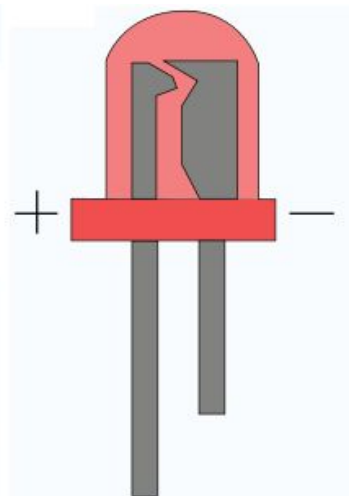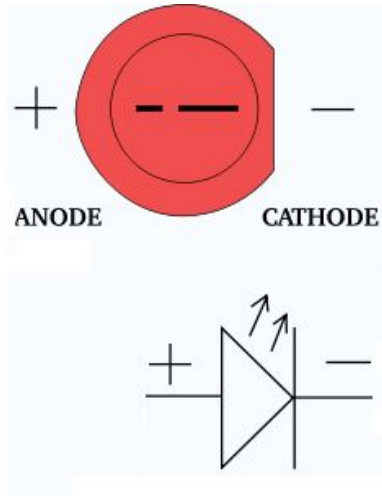
Our network resistor name is "A 102 J".
The "A" means all resistors share one pin.
102 means $1K \Omega$



排阻命名方法			
第一部分電路類型	第二部分引腳數	第三部分阻值	第四部分誤差
A-所有電阻共用一端，公共端從左端（第1引腳）引出 B-每個電阻有各自獨立引腳，相互間無連接 C-各個電阻首尾相連，各連接到均有引出腳 D-所有電阻共用一端，公共端從中間引出 E、F、G、H、I-內部連接較複雜，不常用，此次略去	4~14	3位數字（第1、2位為有效數，第3位為有效數後面0的個數，如102表示1000Ω）	F-±1% G-±2% J-±5%

Negative logic and Positive logic

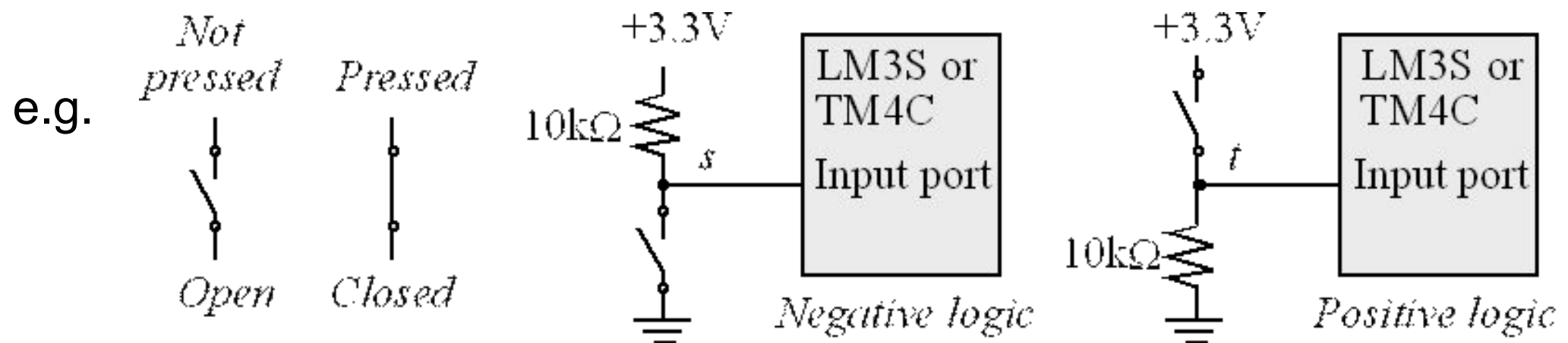- logic can mean to the logical level received by the CPU when a component "action" or "trigger"
- Positive logic or Active High
 - When component actions, CPU receives High level ("1")
- Negative logic or Active Low
 - When component actions, CPU receives Low level ("0")



Hardware Sketch

- <http://fritzing.org/>